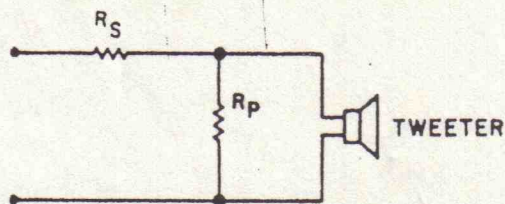


## IMPEDANCE CORRECTED ATTENUATION

Given a too efficient driver, it has previously been a matter of trial and error in trying to find the proper series resistor to match the driver to the system. Once the series resistor was found, most individuals stop; not realizing the major impedance change now in the system. Not only would the change effect passive crossovers, it also effects the transient response of the amplifier. Trying to find both series and pass resistor through trial and error methods would cause anyone hair loss.

Fortunately, there are two simple equations that allow calculation of the proper pass ( $R_p$ ) and series ( $R_s$ ) resistors. Given driver impedance ( $Z_D$ ) and attenuation in negative decibels ( $A$ ), the circuit and formulas are defined as follows:



$$R_p = \frac{10^{(A/20)} Z_D}{1 - 10^{(A/20)}}$$

$$R_s = Z_D - \frac{1}{(1/R_p) + (1/Z_D)}$$

A form of these formulas can be used to find the system equivalent impedance ( $Z_{eq}$ ) and attenuation ( $A$ ) if they are the unknowns. The equations are as follows:

$$Z_{eq} = \frac{1}{(1/R_p) + (1/Z_D)} + R_s$$


$$A = 20 \log \left[ \frac{1}{\frac{(1/R_p) + (1/Z_D)}{Z_{eq}}} \right]$$

Recently, a speaker manufacturer published an attenuation system that was incorrect. The circuit given would drop the driver impedance from 4 ohms to less than 1.5 ohms. Obviously, it could cause drastic problems with regard to both crossover frequency as well as amplifier reliability. This kind of misinformation seems to be an all too common problem. Therefore, please check all published attenuation network values with the previous formulas before using them in systems. It will save us all a lot of headaches!



## Resistor Attenuators

Speaker Impedance	Attenuation	R Parallel	R Series	Resultant Impedance
8	1.02 dB	—	1	9.00
8	1.16 dB	56	1	8.00
8	1.94 dB	—	2	10.00
8	2.48 dB	25	2	8.02
8	2.61 dB	20	2	7.71
8	2.82 dB	15	2	7.22
8	3.23 dB	10	2	6.44
8	3.67 dB	20	3	8.71
8	3.95 dB	15	3	8.22
8	4.48 dB	10	3	7.44
8	5.58 dB	10	4	8.44
8	6.16 dB	7.5	4	7.87
8	7.25 dB	5	4	7.07
8	8.39 dB	5	5	8.07
8	9.17 dB	4	5	7.67
8	12.31 dB	2	5	6.60
8	15.10 dB	2	7.5	9.10
8	16.42 dB	1	5	5.89
8	19.50 dB	1	7.5	8.39

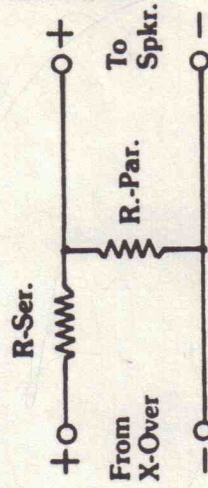

## Capacitor Crossover Points

Eight Ohm Capacitor		Crossover (4.5dB)	
3dB point	12dB point	3dB point	12dB point
2.2 $\mu$ f	9043 Hz	18085 Hz	4522 Hz
3.3 $\mu$ f	6029 Hz	12058 Hz	3014 Hz
4.7 $\mu$ f	4233 Hz	8466 Hz	2166 Hz
6.8 $\mu$ f	2926 Hz	5852 Hz	1463 Hz
10 $\mu$ f	1989 Hz	3978 Hz	995 Hz
15 $\mu$ f	1326 Hz	2652 Hz	663 Hz
22 $\mu$ f	904 Hz	1808 Hz	452 Hz
33 $\mu$ f	603 Hz	1206 Hz	301 Hz
47 $\mu$ f	423 Hz	846 Hz	212 Hz
100 $\mu$ f	199 Hz	399 Hz	100 Hz

Four Ohm Capacitor		Crossover (4.5dB)	
3dB point	12dB point	3dB point	12dB point
2.2 $\mu$ f	9043 Hz	18085 Hz	4522 Hz
3.3 $\mu$ f	6029 Hz	12058 Hz	3014 Hz
4.7 $\mu$ f	4233 Hz	8466 Hz	2166 Hz
6.8 $\mu$ f	2926 Hz	5852 Hz	1463 Hz
10 $\mu$ f	1989 Hz	3978 Hz	995 Hz
15 $\mu$ f	1326 Hz	2652 Hz	663 Hz
22 $\mu$ f	904 Hz	1808 Hz	452 Hz
33 $\mu$ f	603 Hz	1206 Hz	301 Hz
47 $\mu$ f	423 Hz	846 Hz	212 Hz
100 $\mu$ f	199 Hz	399 Hz	100 Hz



# THE BUSINESS OF MOBILE AUDIO

By John Patterson, President of PAC

Editor's Note: PAC may be contacted at (800) 854-3133 for assistance with crossovers or a catalog.



Resistors in a speaker circuit are useful to reduce the amount of power a speaker receives. If a speaker or speakers are to be used for rear fill, the power going to that circuit may be desired at a reduced level. In some instances, a particular speaker may be too loud and create an unbalanced system.

Tweeters and other small speakers may need protection and usually can afford a reduced amount of power. A single speaker used for center imaging may have both the right and left channel input to it and, in most instances, resistors are necessary to stabilize the load an amplifier sees in that section.

If a passive crossover is made for a particular ohm load which is not the same as the speaker, a resistor can be used to change the ohm load seen by the crossover. Resistors may be used in series or in parallel with a speaker.

What happens to the amount of power which ends up driving the speaker when a resistor is used is similar to what happens when two speakers are put in series or in parallel. The essential difference between a speaker and resistor is a resistor turns its power into heat rather than music.

## SERIES RESISTORS

Series resistors will always reduce the power which reaches the speaker. The

amount of power ending up at the speaker is dependent on two factors:

- 1) The change in amplifier load, and
- 2) The distribution of power between the resistor and the speaker.

As an example, a 4 ohm resistor in series with a 4 ohm speaker will double the amplifier load and in theory reduce amplifier output by 50 %. In practice, most amplifier circuits will respond with a slightly increased output into this increased load. As a general rule, the amplifier output will be 60% rather than 50 %.

The reduced amplifier output is then split evenly between the

speaker and resistor. Therefore the speaker receives 1/2 of the 60 % of power or 30 % of the original amplifier power. The 30 % powering the resistor helps heat the car.

To figure various resistor and speaker value combinations use the formula or chart shown below.


When a resistor is used in a passive crossover circuit, the value of coils and/or capacitors need to be chosen based on the ohm load of the speaker and resistor combination. Two 4 ohm speakers in series would require an 8 ohm crossover. A 4 ohm resistor in series with a 4 ohm speaker would also require an 8 ohm crossover. More on resistors in March.

## FORMULA AND CHART RESISTOR AND SPEAKER IN SERIES

$$1 / \left( \frac{R1 + R2}{R2} \right) \times \left( \frac{R2}{R1 + R2} \right) = \text{POWER TO SPEAKER}$$

Not adjusted for the small increase in power from the amplifier circuitry.

### SERIES RESISTOR

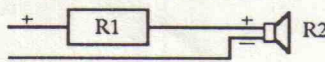

## % OF POWER RECEIVED BY SPEAKER WITH RESISTOR IN SERIES

RESISTOR OHMS	S P E A K E R O H M S			
	3	4	6	8
1	56	64	73	79
2	36	44	56	64
3	25	33	44	53
4	18	25	36	44
6	11	16	25	33
8	7	11	18	25